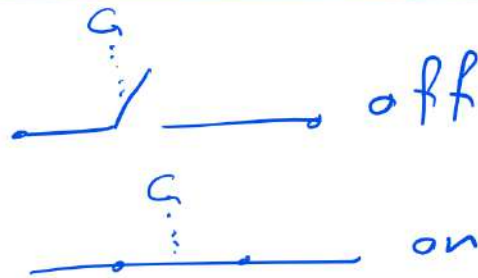


L #1


1819 w ALG

①

Transistor $\begin{cases} \rightarrow 1 - \text{switch} \\ \rightarrow 2 - \text{Resistor} \end{cases}$




* AND logic
(series)

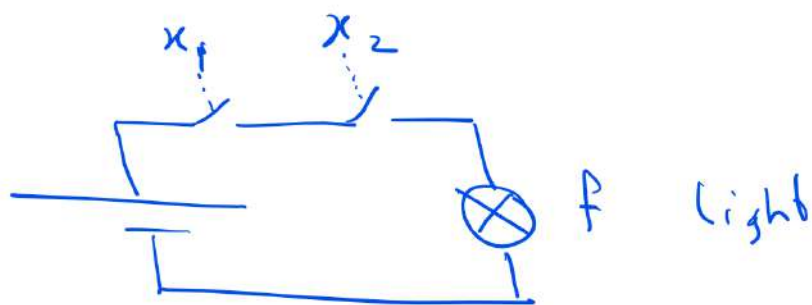

$$f(x_1, x_2) = x_1 \cdot x_2$$

$\downarrow$
AND

* OR logic (parallel)

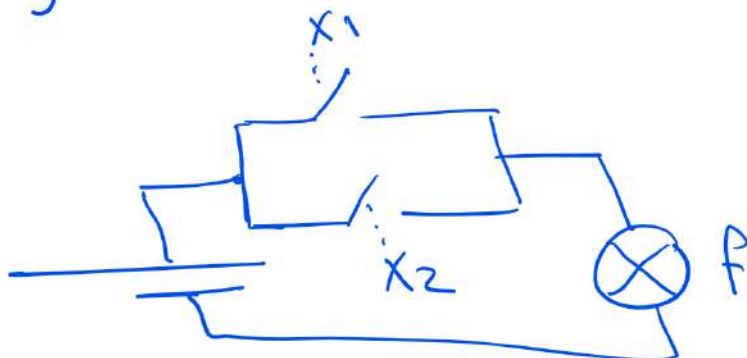


$$f(x_1, x_2) = x_1 + x_2$$

$\downarrow$
OR

NOT Logic (inverter)

(2)

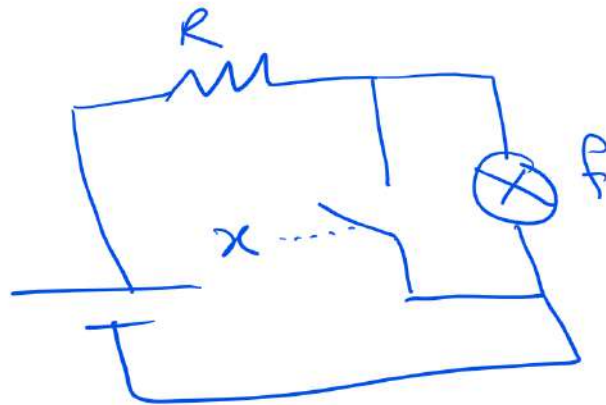


if $x = \underline{1}$ (on) $\rightarrow f = \underline{0}$ off
 $x = \underline{0}$ (off) $\rightarrow f = \underline{1}$ on

$$\left. \begin{aligned} f(x) &= \bar{x} \\ &= \sim x \\ &= x' \end{aligned} \right\} \text{NOT}$$

Gate / Truth table


⑤ AND gate

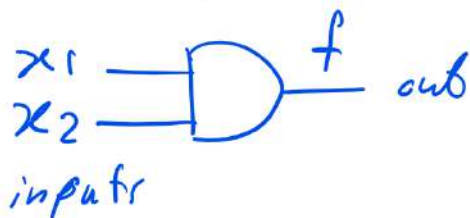

x_1	x_2	f
0	0	0
0	1	0
1	0	0
1	1	1

$$\left. \begin{aligned} f(x_1, x_2) &= x_1 \cdot x_2 \\ &= x_1 x_2 \end{aligned} \right\}$$


② OR gate

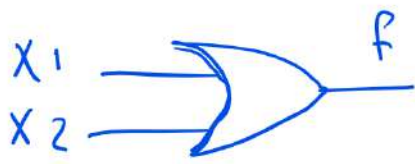

$$f(x_1, x_2) = x_1 + x_2$$

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1


③ NOT gate

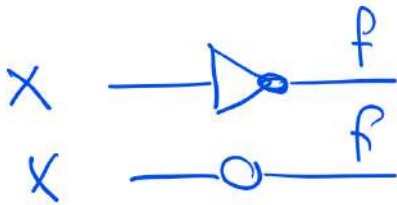

x	f
0	1
1	0

$$f(x) = \bar{x}$$


④ NAND (AND - NOT)

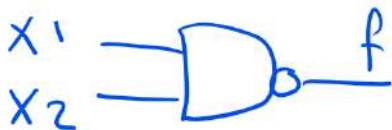

$$f(x_1, x_2) = \overline{x_1 \cdot x_2}$$

x_1	x_2	f
0	0	1
0	1	1
1	0	1
1	1	0

⑤ NOR gate (OR - NOT)

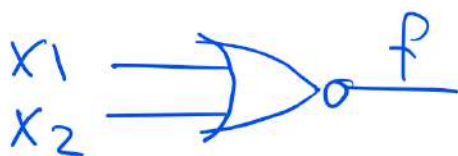


$$f(x_1, x_2) = \overline{x_1 + x_2}$$

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0

(4)

⑥ XOR : exclusive OR gate

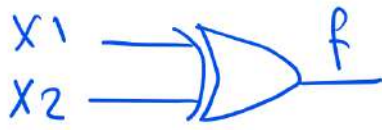

$$f(x_1, x_2) = x_1 \oplus x_2$$

$$= \underline{\overline{x_1}} \cdot \underline{x_2} + \underline{x_1} \cdot \underline{\overline{x_2}}$$

مختلفين

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	0

⑦ XNOR : XOR - NOT



$$f(x_1, x_2) = \overline{x_1 \oplus x_2}$$

$$= \underline{\overline{x_1}} \cdot \underline{\overline{x_2}} + \underline{x_1} \cdot \underline{x_2}$$

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	1

$$\overset{\text{XNOR}}{\downarrow}$$

$$x_1 \odot x_2 = \overline{x_1 \oplus x_2}$$

$$= \underline{\overline{x_1}} \cdot \underline{\overline{x_2}} + \underline{x_1} \cdot \underline{x_2}$$

of rows = 2^n ; n = # of variables (inputs)



$$n = 2 \rightarrow \text{row} = 2^2 = 4$$

$$n = 3 \rightarrow \text{row} = 2^3 = 8$$

Truth table: is used to show the functional behavior of the circuit.


(5)

Draw the following circuit using gates

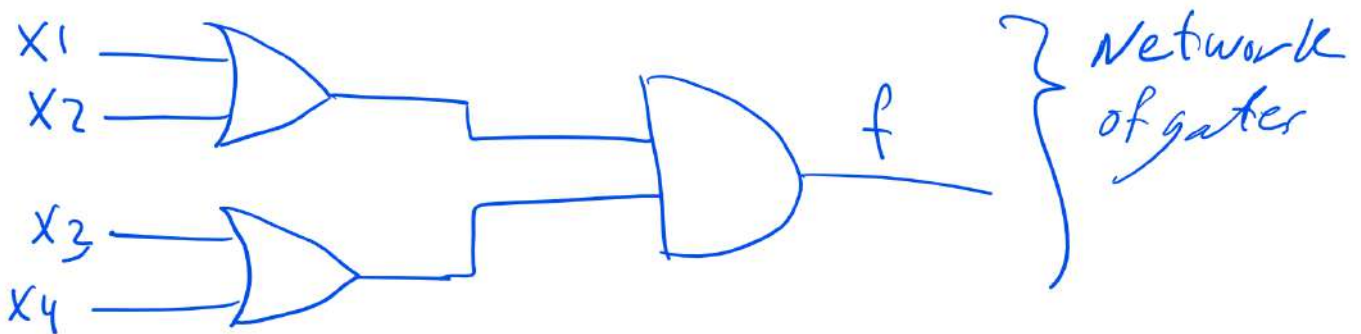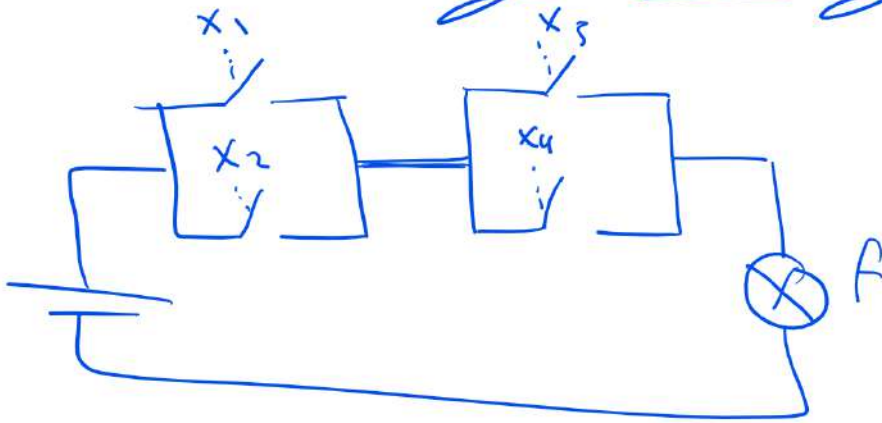

$$f(x_1, x_2, x_3, x_4) = (x_1 + x_2) \cdot (x_3 + x_4)$$


Example I: Given the following

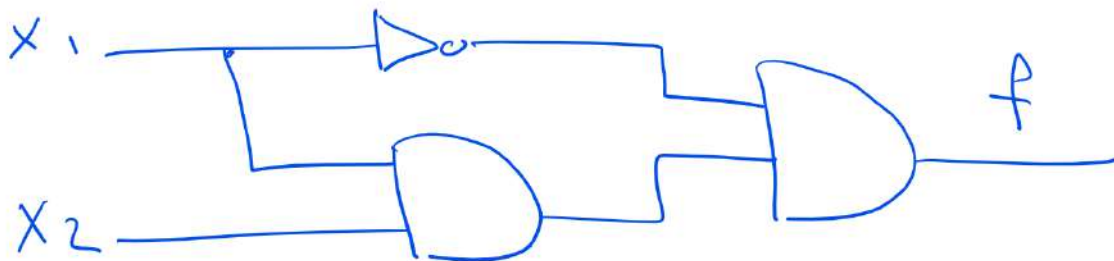

- 1- what is the function of the circuit
- 2- Draw truth table ^{Logical expression} ?

3- what is the cost of the circuit?

4- Draw timing diagram?

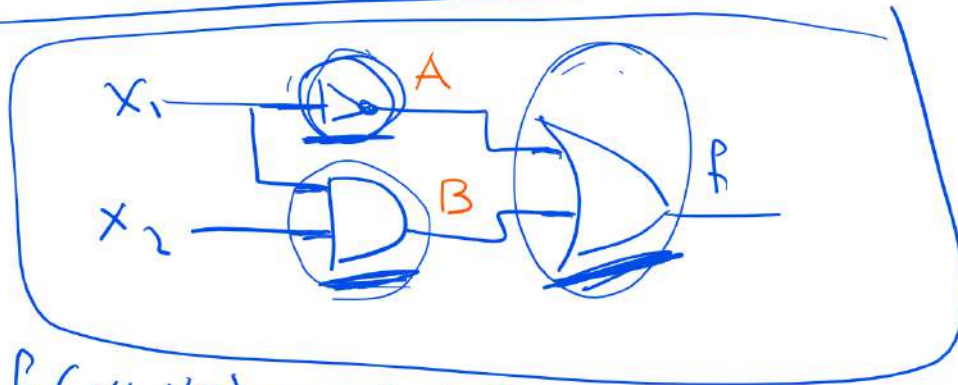

$$f(x_1, x_2) = A + B$$

$$= \overline{x_1} + B$$

$$F = \overline{x_1} + x_1 \cdot x_2$$

2- Truth table


x_1	x_2	A	B	f
0	0	1	0	1
0	1	1	0	1
1	0	0	0	0
1	1	0	1	1

3- Cost : # of gates
+ inputs for gates

$$\text{Cost} = 3 + 5 = 8$$

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1


4. Timing diagram:

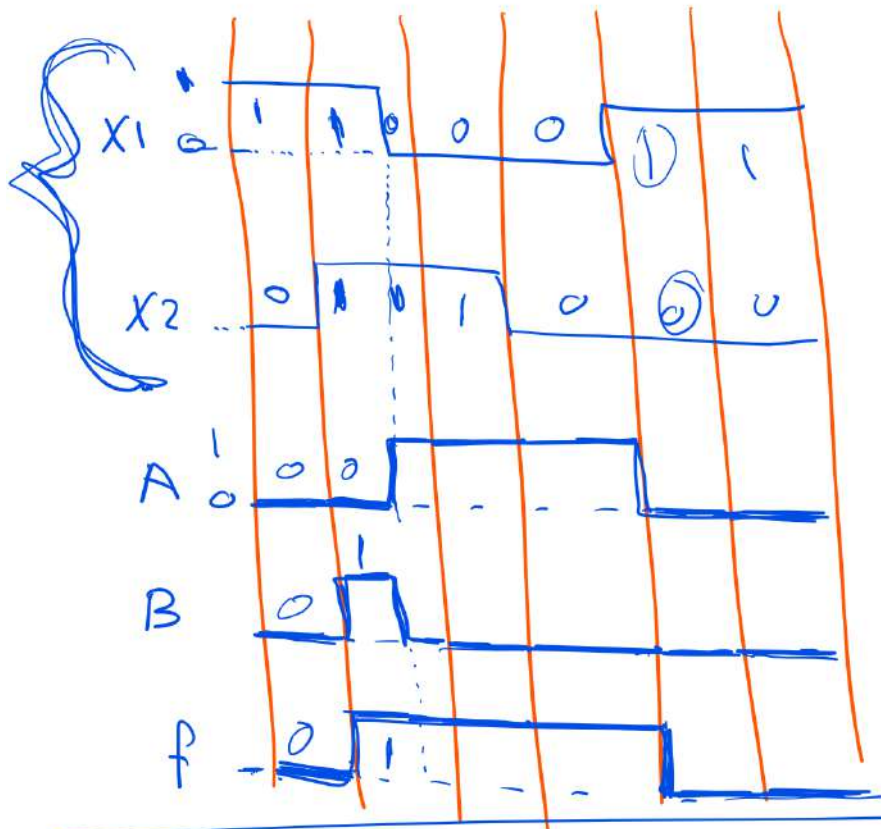


⑦

X ₁	X ₂	A	B	F
0	0	1	0	1
0	1	1	0	1
1	0	0	0	0
1	1	0	1	1

Example II: Given the following circuit

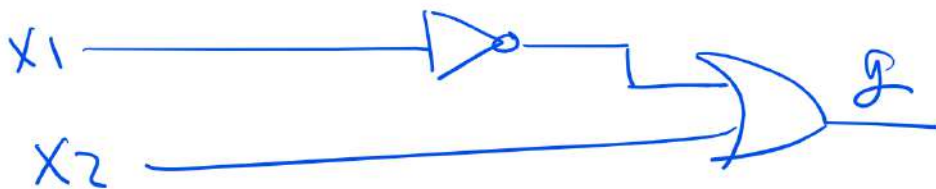

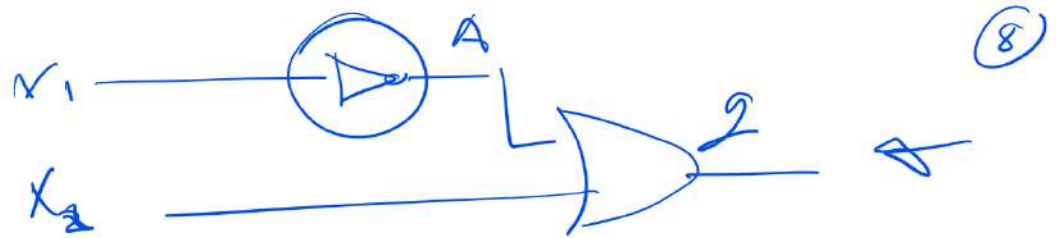1. Derive the logical expression
2. Draw truth table
3. What is the cost of the circuit?



1. $f(X_1, X_2) = A + X_2$

$g = \overline{X_1} + X_2$

2. Truth table

X_1	X_2	A	g
0	0	1	1
0	1	1	1
1	0	0	0
1	1	0	1

3. cost = 2 + 3 = 5

$f = g$ The two circuits are functionally equivalent

$\overline{X_1} + X_1 \cdot X_2 = \overline{X_1} + X_2$

we can prove that $f = g$ in two ways

1- Truth table

2- Boolean algebra

I - Axioms:

2

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

$$0 + 0 = 0$$

$$0 + 1 = 1 + 0 = 1$$

$$1 + 1 = 1$$

$$\overline{0} = 1$$

$$\overline{1} = 0$$

II - One variable

$$\underline{x} \cdot \underline{0} = 0$$

$$x + 0 = x$$

$$x \cdot 1 = x$$

$$x + 1 = 1$$

$$x \cdot x = x$$

$$x + x = x$$

$$x \cdot \overline{x} = 0$$

$$x + \overline{x} = 1$$

$$\overline{\overline{x}} = x$$

III - Two or three variables

$$1- x \cdot y = y \cdot x \xrightarrow{\text{dual}} x + y = y + x$$

$$2- x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

$$\hookrightarrow x + (y + z) = (x + y) + z$$

$$3- x \cdot (y + z) = x \cdot y + x \cdot z$$

$$4- x + x \cdot y = x \xrightarrow{\text{dual}} x \cdot (x + y) = x$$

$$5- x \cdot y + x \cdot \bar{y} = x \xrightarrow{\text{dual}} (x + y) \cdot (x + \bar{y}) = x$$

$$6- \overline{x \cdot y} = \bar{x} + \bar{y} \quad \text{De Morgan's Law}$$

$$\hookrightarrow \overline{x + y} = \bar{x} \cdot \bar{y}$$

$$7- \underline{x} + \underline{\bar{x}} \cdot y = x + y$$

$$8- \underline{x} \cdot y + y \cdot \underline{z} + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$$

$$\hookrightarrow (x + y) \cdot (y + z) \cdot (\bar{x} + z) = (x + y) \cdot (\bar{x} + z)$$

* principle of duality

$$x \cdot 0 = 0$$

dual

$$x + 1 = 1 \checkmark$$

(11)

Given logical expression:
 replace each $\cdot$ with $+$ and vice versa
 and 1 with 0 and 0 with 1
 you will get a new logical expression

minimize the following expression using
 Boolean algebra

$$\begin{aligned}\overline{x_1}x_2 + x_1\overline{x_2} + \overline{x_1}\overline{x_2} &= \\ &= \overline{x_1}(x_2 + \overline{x_2}) + x_1\overline{x_2} \\ &= \overline{x_1}(1) + x_1\overline{x_2} \\ &= \overline{x_1} + x_1\overline{x_2} \\ &= \overline{x_1} + \overline{x_2}\end{aligned}$$

یا سو

$$\underline{xy} + \underline{x\overline{y}} = x$$

$$\begin{aligned}\overline{x_1}x_2 + x_1\overline{x_2} + \overline{x_1}\overline{x_2} &= \overline{x_2} + \overline{x_1}x_2 \\ &= \overline{x_2} + \overline{x_1}\end{aligned}$$

(12)

prove that:

$$\underbrace{X + Y \cdot Z}_{LHS} = \underbrace{(X + Y) \cdot (X + Z)}_{RHS}$$

$$RHS = (X + Y) \cdot (X + Z)$$

$$= X \cdot X + X \cdot Z + Y \cdot X + Y \cdot Z$$

$$= \underbrace{X}_{\downarrow} + \underbrace{XZ}_{\downarrow} + YX + YZ$$

$$= \underbrace{X + YX}_{\downarrow} + YZ$$

$$= X + Y \cdot Z = LHS$$

Example: prove that

$$\underbrace{ab + \bar{a}c + bc}_{LHS} = \underbrace{ab + \bar{a}c}_{RHS}$$

$$LHS = ab + \bar{a}c + \underline{bc}$$

$$= ab + \bar{a}c + (1 \cdot bc)$$

$$= ab + \bar{a}c + (a + \bar{a})bc$$

$$= \underbrace{ab + abc}_{\downarrow} + \underbrace{\bar{a}c + \bar{a}bc}_{\downarrow}$$

$$= ab + \bar{a}c = RHS$$

$$\underline{ab + \bar{a}c + bc} = \underline{ab + \bar{a}c}$$

$$LHS = ab + \bar{a}c + bc$$

$$= ab1 + \bar{a}1c + 1bc$$

$$= ab(c + \bar{c}) + \bar{a}(b + \bar{b})c + (a + \bar{a})bc$$

$$= \underline{abc} + \underline{ab\bar{c}} + \underline{\bar{a}bc} + \underline{\bar{a}\bar{b}c} + \underline{abc} + \underline{\bar{a}bc}$$

$$= \underline{abc} + \underline{ab\bar{c}} + \underline{\bar{a}bc} + \underline{\bar{a}\bar{b}c}$$

$$RHS = ab + \bar{a}c$$

$$= ab(c + \bar{c}) + \bar{a}(b + \bar{b})c$$

$$= \underline{abc} + \underline{ab\bar{c}} + \underline{\bar{a}bc} + \underline{\bar{a}\bar{b}c}$$

$$= LHS$$

prove that:

(14)

$$\underline{(X_1 + X_2 + X_3) \cdot (X_1 + X_2 + \bar{X}_3) \cdot (X_1 + \bar{X}_2 + X_3) \cdot (X_1 + \bar{X}_2 + \bar{X}_3)}$$

$$\cdot \underline{(\bar{X}_1 + X_2 + X_3) \cdot (\bar{X}_1 + X_2 + \bar{X}_3) \cdot (X_1 + X_2 + \bar{X}_3)} = \underline{X_1 X_2}$$

$$LHS = (X_1 + X_2) \cdot (\bar{X}_1 + X_2) \cdot (X_1 + \bar{X}_3) \cdot (X_1 + \bar{X}_2 + X_3)$$

$$= X_2 \cdot (X_1 + \bar{X}_3) \cdot (X_1 + \bar{X}_2 + X_3)$$

$$= X_2 \cdot X_1 + (\bar{X}_3 \cdot \bar{X}_2 + X_3)$$


$$= X_2 \cdot X_1 + (\bar{X}_3 \cdot \bar{X}_2)$$

$$= X_2 \cdot (X_1 + \bar{X}_3) \cdot (X_1 + \bar{X}_2)$$

$$= X_2 \cdot X_1 \cdot (X_1 + \bar{X}_3)$$

$$= X_2 \cdot X_1$$

$$= X_1 \cdot X_2 = RHS$$

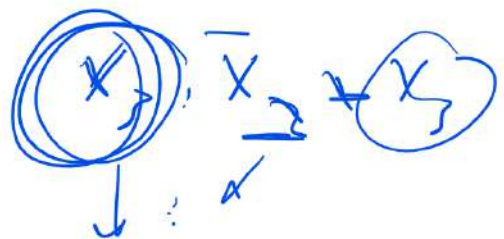

$$\underline{a \cdot b} = \bar{a} + b$$